 


Combinational Logic Applications

ECE2300L Module 3 Report



Kyler Martinez
October 21st, 2020

Introduction

The learning objectives of the module include designing a code converter using combinations of components such as encoders, decoders, multiplexors, and arithmetic circuits. Students will also learn how to compare unsigned binary numbers and signed number in sign-magnitude/2's complement representations. Finally, to get the skills to be able to analyze a half/full adder and assemble a multi-bit add/subtract circuit with overflow detection logic.

Activity 3.1 — Binary To BCD Converter

Truth Table For Binary To BCD Converter

Decimal	Binary B ₃ B ₂ B ₁ B ₀	BCD D ₄ D ₃ D ₂ D ₁ D ₀	Adjusted A ₃ A ₂ A ₁ A ₀
0	0000	0 0000	0000
1	0001	0 0001	0001
2	0010	0 0010	0010
3	0011	0 0011	0011
4	0100	0 0100	0100
5	0101	0 0101	0101
6	0110	0 0110	0110
7	0111	0 0111	0111

Decimal	Binary B ₃ B ₂ B ₁ B ₀	BCD D ₄ D ₃ D ₂ D ₁ D ₀	Adjusted A ₃ A ₂ A ₁ A ₀
8	1000	0 1000	1000
9	1001	0 1001	1001
10	1010	1 0000	0000
11	1011	1 0001	0001
12	1100	1 0010	0010
13	1101	1 0011	0011
14	1110	1 0100	0100
15	1111	1 0101	0101

Table 1: Truth Table For Binary To BCD Converter

 


Figure 1: Block Diagram Of The Logic Circuit

- A. $A_0 = B_0$, $A_1 = B_1$, $A_2 = (B_2)(B_1)$, $A_3 = 0$ when $D_4 = 1$, else $A_0 = B_0$, $A_1 = B_1$, $A_2 = B_2$, $A_3 = B_3$
 B.

To reduce the amount of words on the diagram the following variables are used.
 $X = \text{SN74LS00}$ $Y = \text{SN74LS157N}$ $Z = \text{SN74LS08}$ $a = \text{SN74LS47}$
 $B = \text{LTS-64606}$

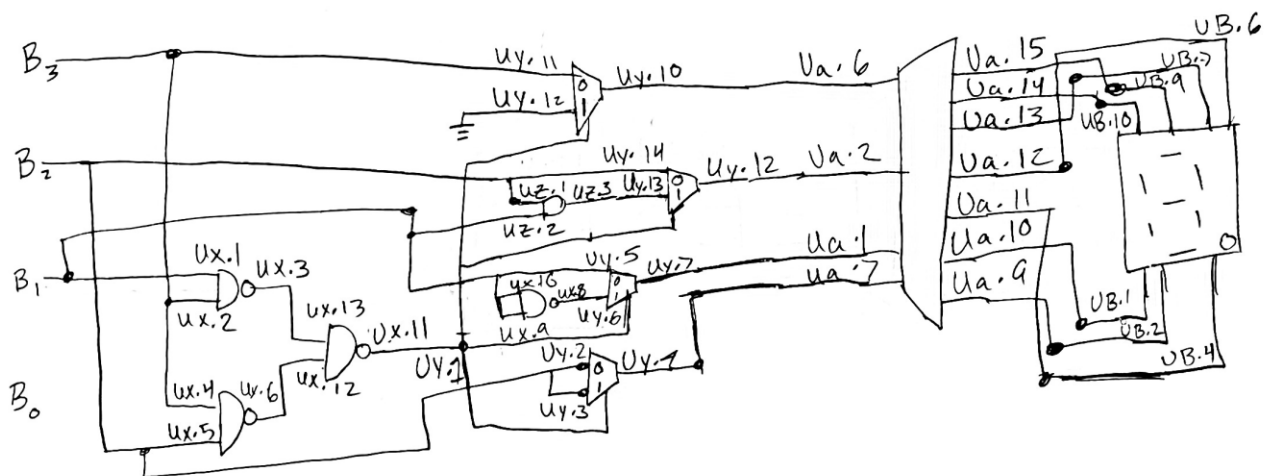


Figure 2: Wiring Diagram

C. Link To Video Demo: <https://youtu.be/HZQJOI6bDo8>

Activity 3.2 — Half Adder/Full Adder

Truth Table For Half Adder

A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C_{out} = AB$$

$$S = A \oplus B$$

Truth Table For Full Adder

C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C_{out} = AB + C_{in}(A+B) = AB + C_{in}(A) + C_{in}(B)$$

$$S = A \oplus B \oplus C_{in}$$

Table 3: Truth Tables For Adders

A.

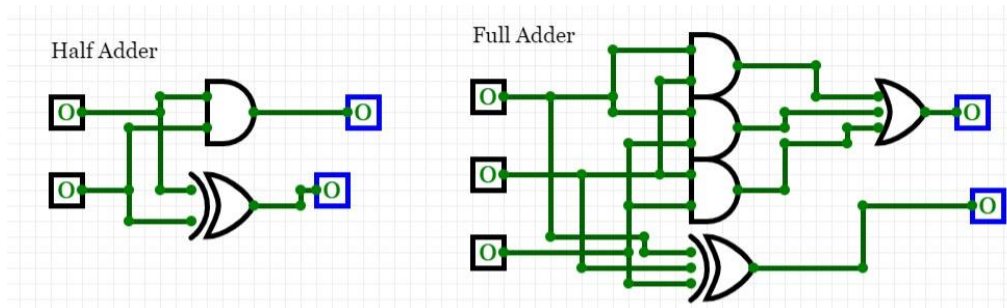


Figure 4: CircuitVerse Diagrams for Adders

B.

To design a circuit to count the number of 1's in a 5-bit input it would not be the best idea to use traditional tools like K-maps and truth tables to develop the logic. This is due to the fact that it would take a long time to list out every possible input combination and the corresponding outputs. It would then take much longer to create 5 variable K-maps for each output and would make it difficult to expand the circuit to include higher bits.

C.

We could use half and full adders to design the circuit since the adders can be used to add the number of 1's in the input. The five input can be broken into two segments, a three bit and a two bit and use a half adder to find the number of 1's in the two bit and the full adder to find the number of 1's in the three bit segment. One way to complete the circuit is to use a half adder with the sum outputs of the half and full adder. The output of the sum adder of this half adder will then be the least significant bit for our total of 1's since we added bits that were in the least significant positions. Then the carry from all the adders will go through a full adder and result in the most significant bit and the middle significant bit. Another solution is to use two full adders and begin with the sum outputs of the two and an input set to ground for the first one and then the sum of this first full adder will be the least significant bit and then if the carry is brought into another full adder the carries from the original half and full adder can be used and result in the most and second most significant bit. Both of these implementations achieve the same end result but are implemented slightly differently.

D..



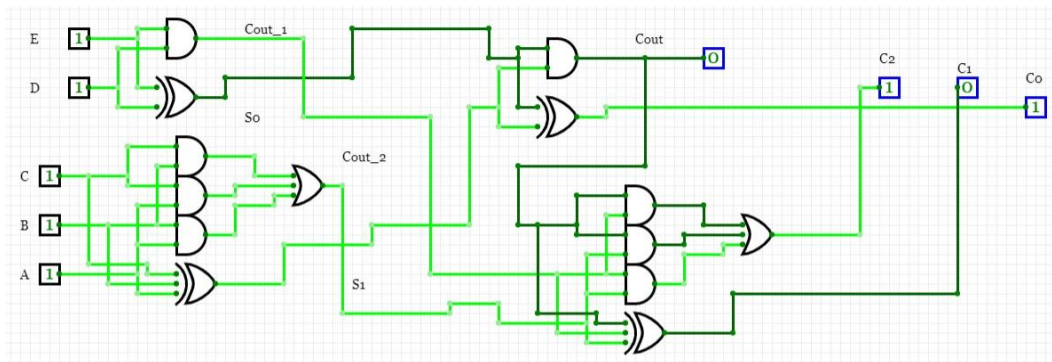


Figure 5: CircuitVerse diagram that counts the 1's in a 5-bit input

E.

Images of simulated circuit with various inputs

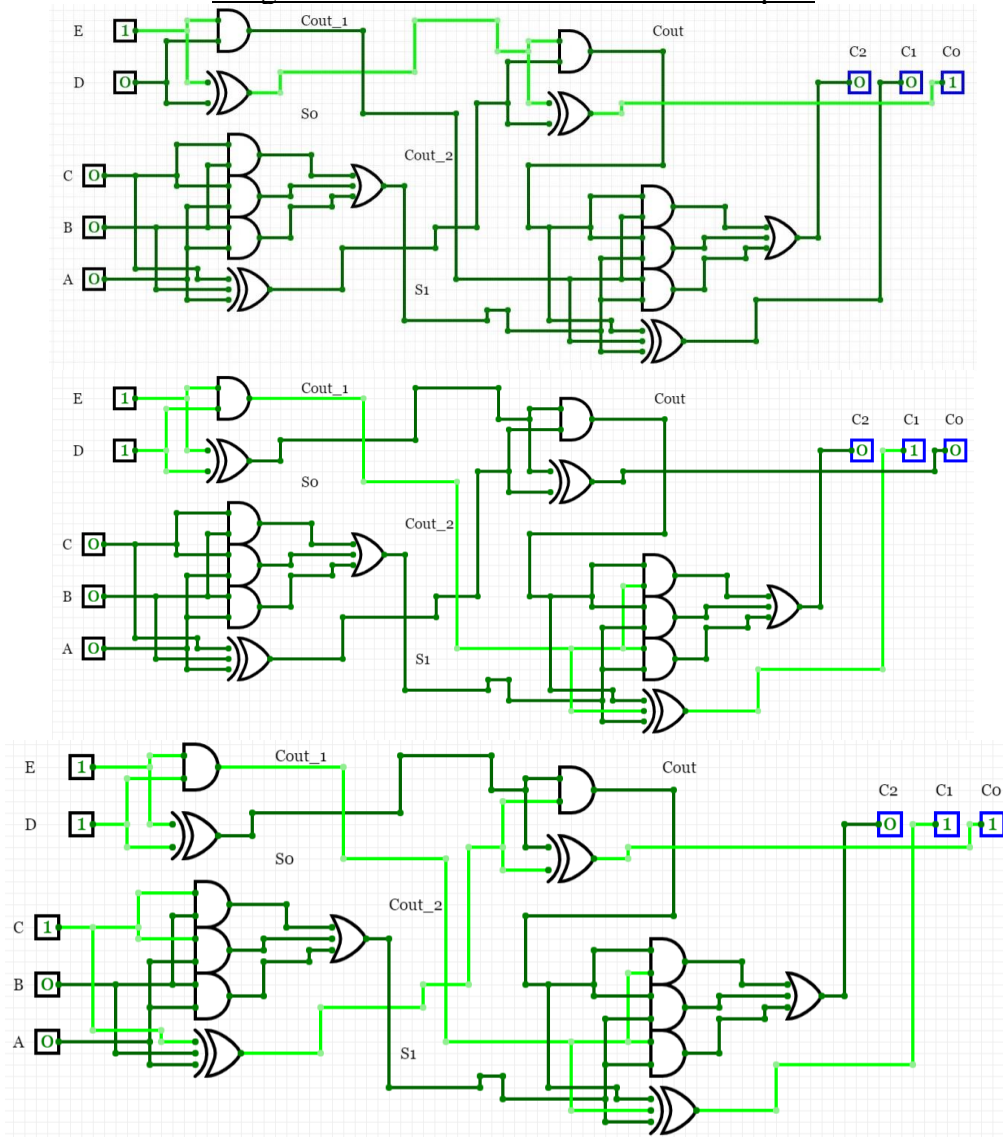

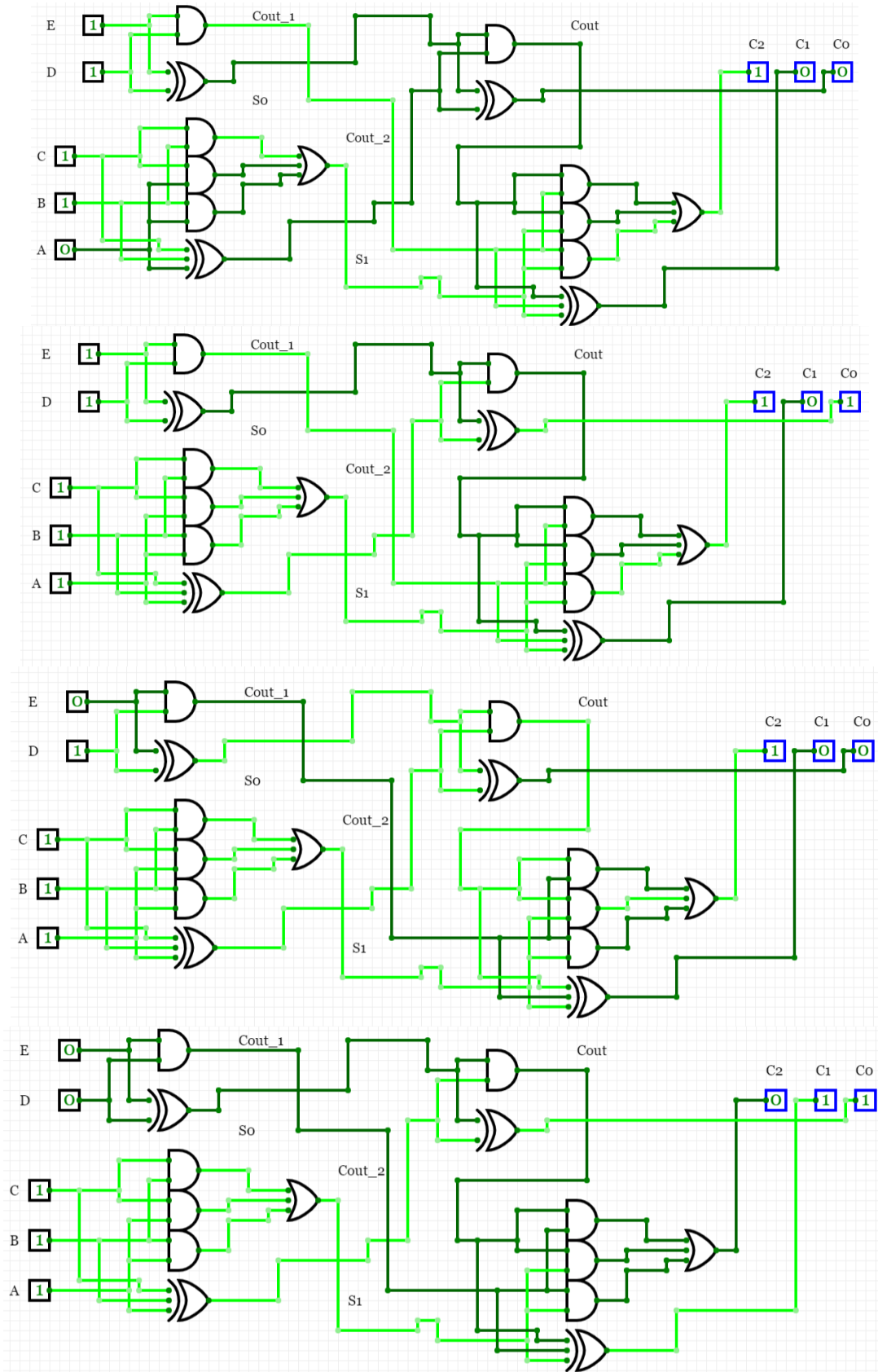

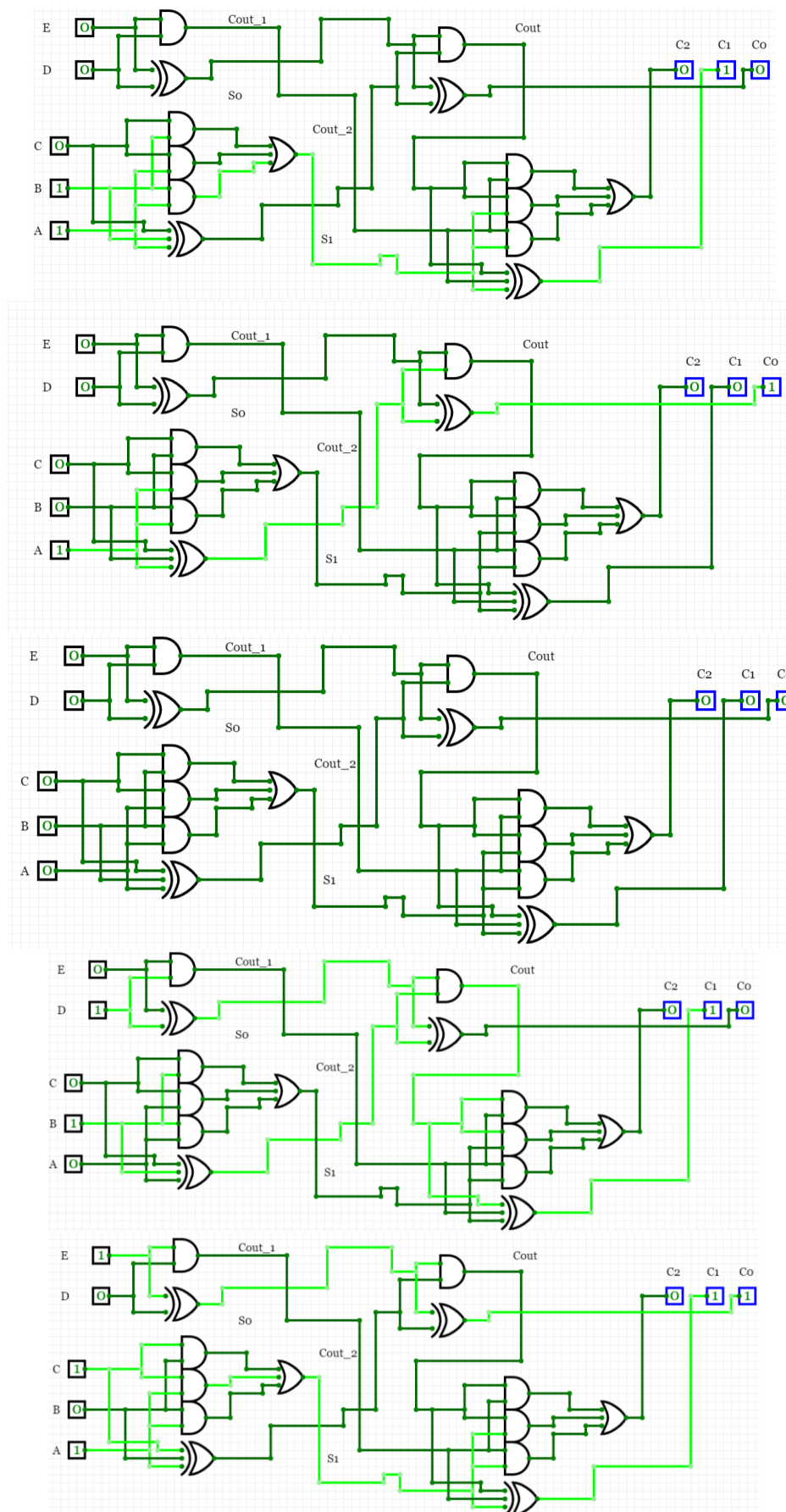


Figure 6: Capture of circuit with different input combinations

Activity 3.3 — Iterative Comparator

A.

in_gt	in_eq	in_lt	p	q	out_gt	out_eq	out_lt
0	0	0	0	0	0	0	0
0	0	1	x	x	0	0	1
0	1	0	0	0	0	1	0
0	1	0	0	1	0	0	1
0	1	0	1	0	1	0	0
0	1	0	1	1	0	1	0
1	0	0	x	x	1	0	0

Table 4: Truth table for single bit comparator

B.

Logic expressions for the table above:

$$\text{out_gt} = \text{in_gt} + (\text{in_eq})(p)(q')$$

$$\text{out_eq} = (\text{in_eq})(p')(q') + (\text{in_eq})(p)(q)$$

$$\text{out_lt} = \text{in_lt} + (\text{in_eq})(p')(q)$$

C.

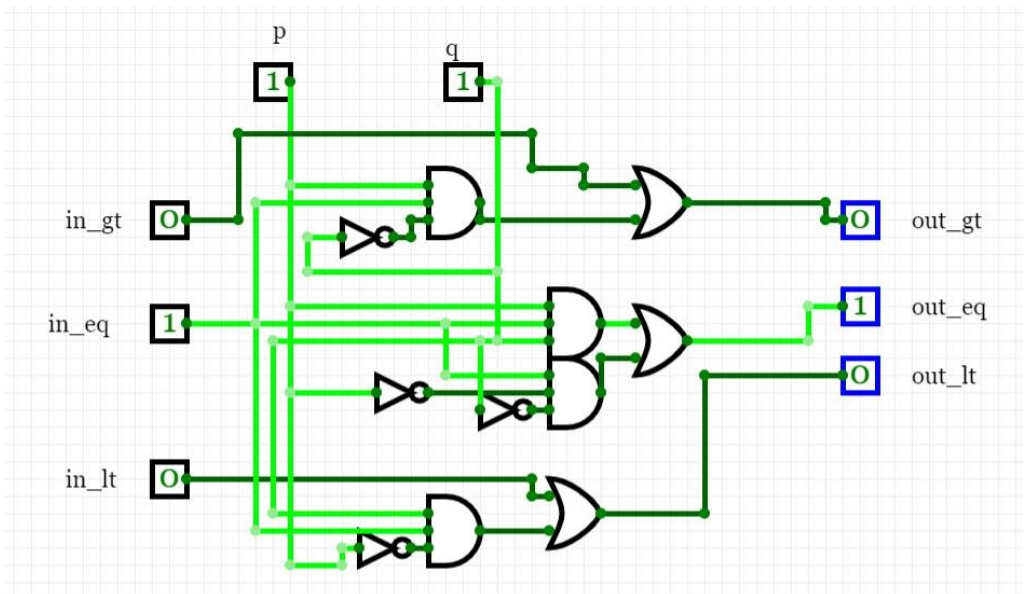


Figure 7: Single bit comparator using CircuitVerse

D.

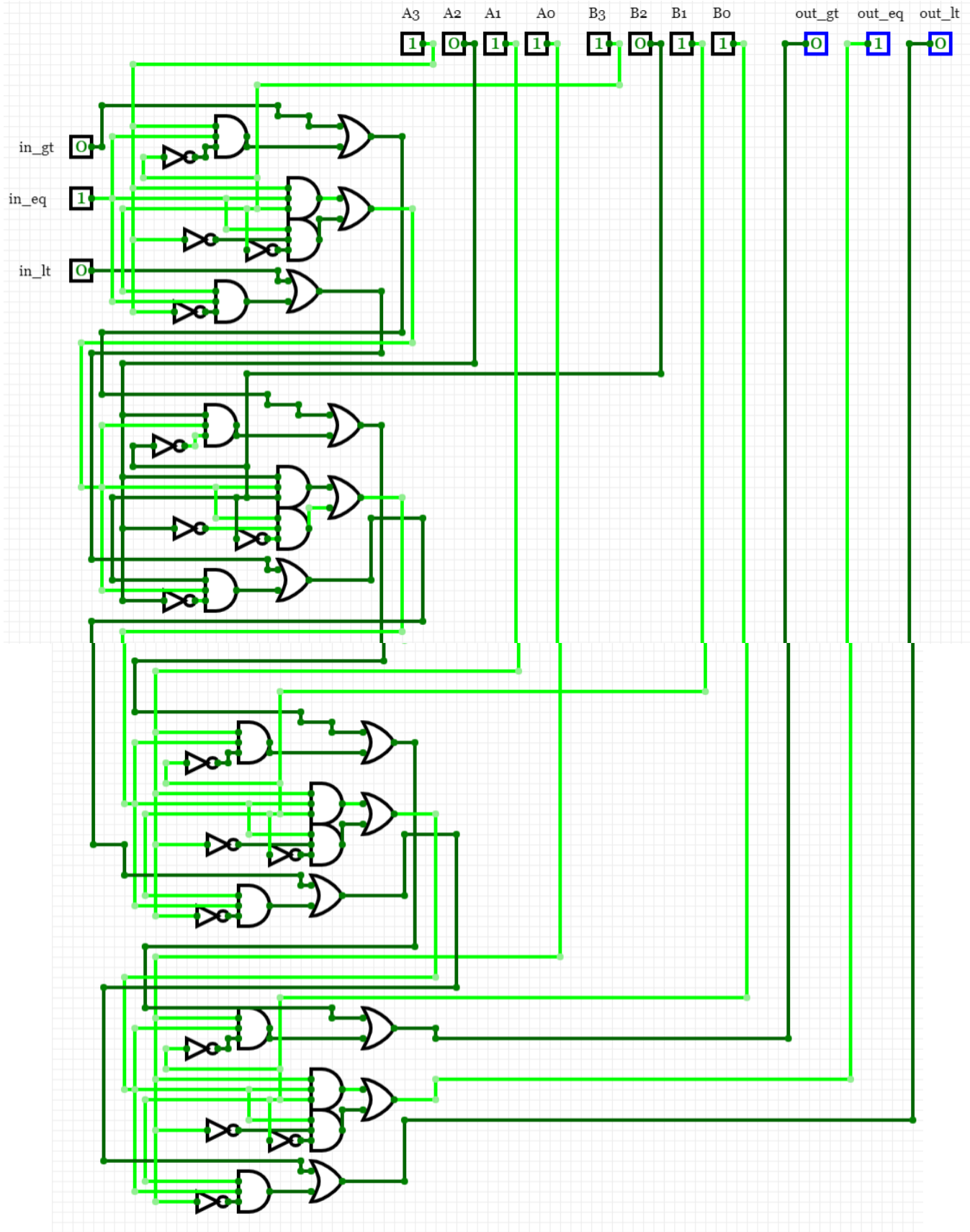



Figure 8: Cascading 4-bit magnitude comparator

E.


Screen shots with various input combinations.

Note: Due to the size of the circuit I only took pictures where any inputs and outputs are visible to decrease the size of the report.

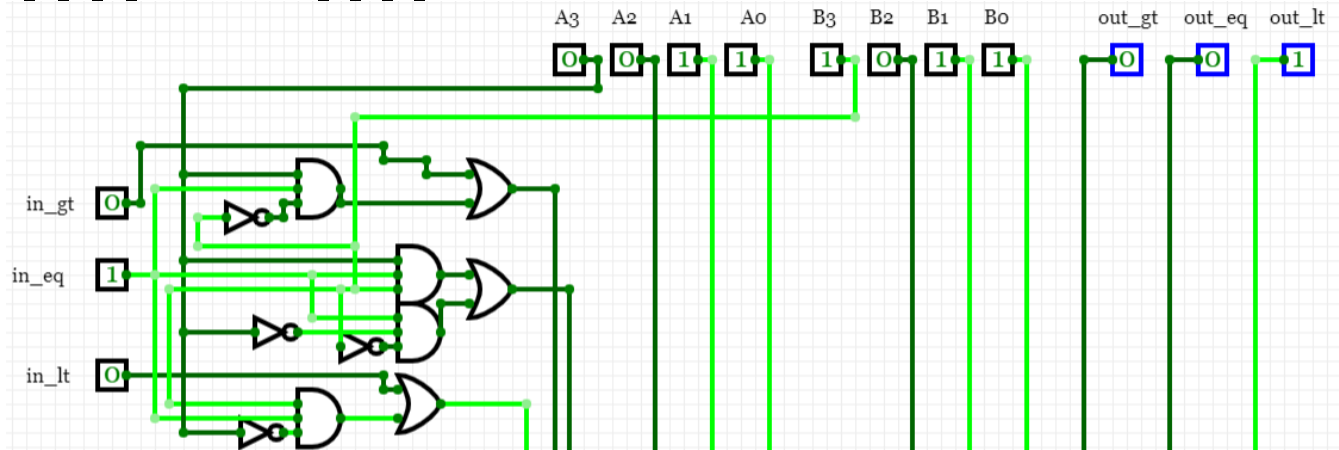
$A_3A_2A_1A_0 = 0xxx$ and $B_3B_2B_1B_0 = 1xxx$



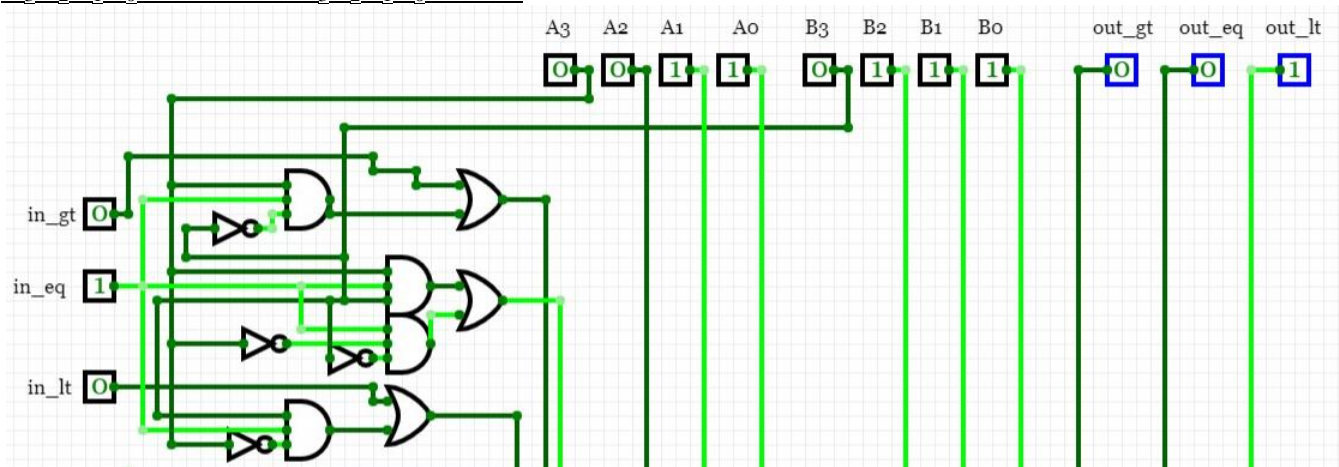
$A_3A_2A_1A_0 = 00xx$ and $B_3B_2B_1B_0 = 01xx$



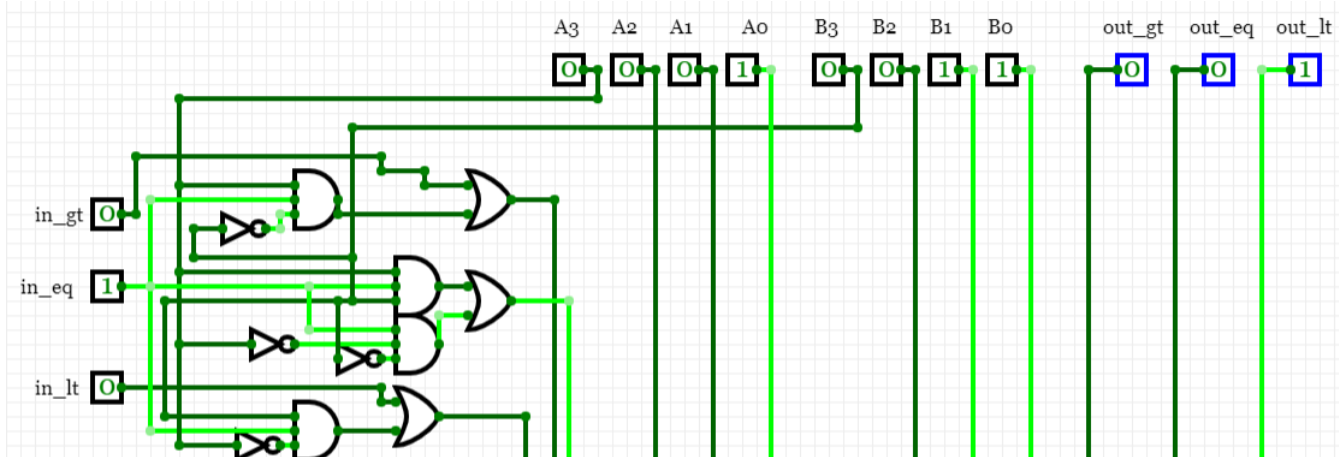
$A_3A_2A_1A_0 = 000x$ and $B_3B_2B_1B_0 = 001x$



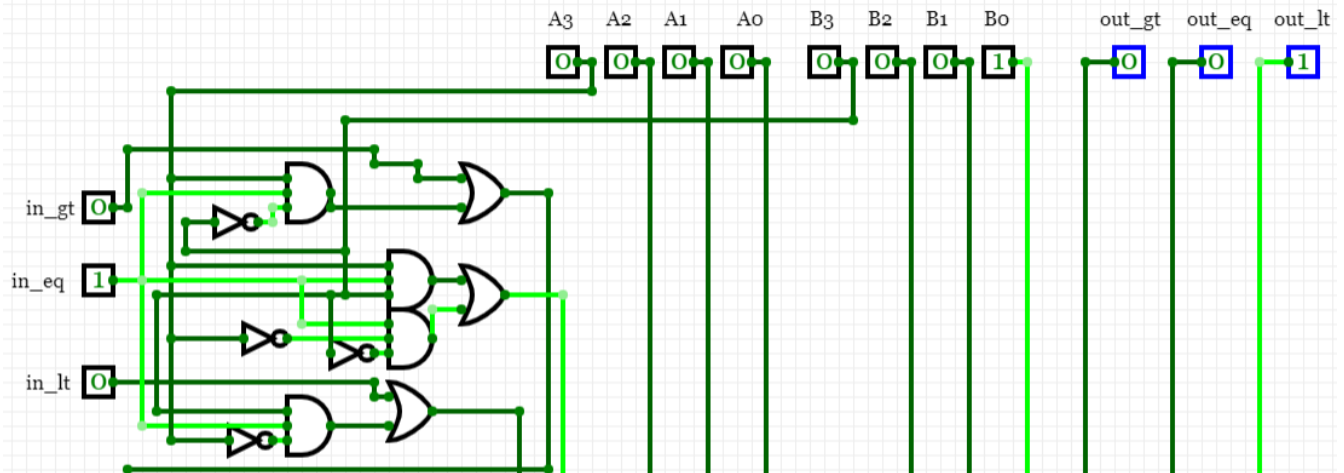
$A_3A_2A_1A_0 = 0000$ and $B_3B_2B_1B_0 = 0001$



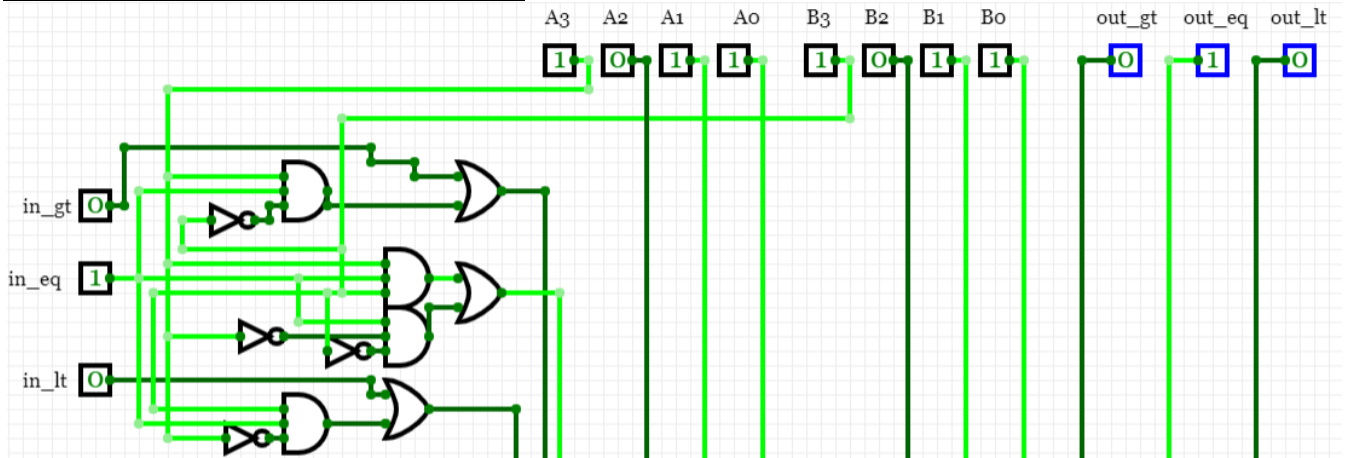
$A_3A_2A_1A_0 = 1011$ and $B_3B_2B_1B_0 = 1011$



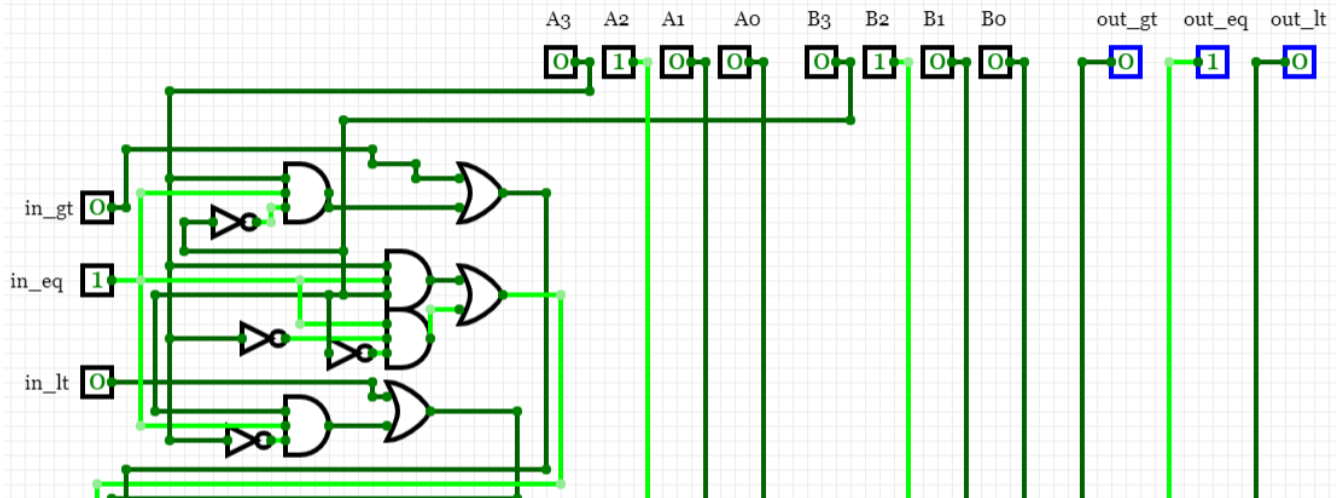
$A_3A_2A_1A_0 = 0100$ and $B_3B_2B_1B_0 = 0100$



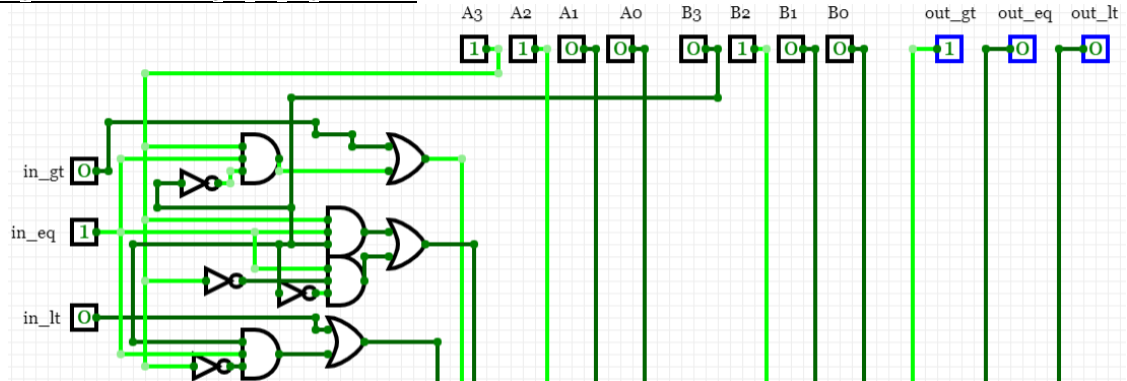
$A_3A_2A_1A_0 = 1xxx$ and $B_3B_2B_1B_0 = 0xxx$



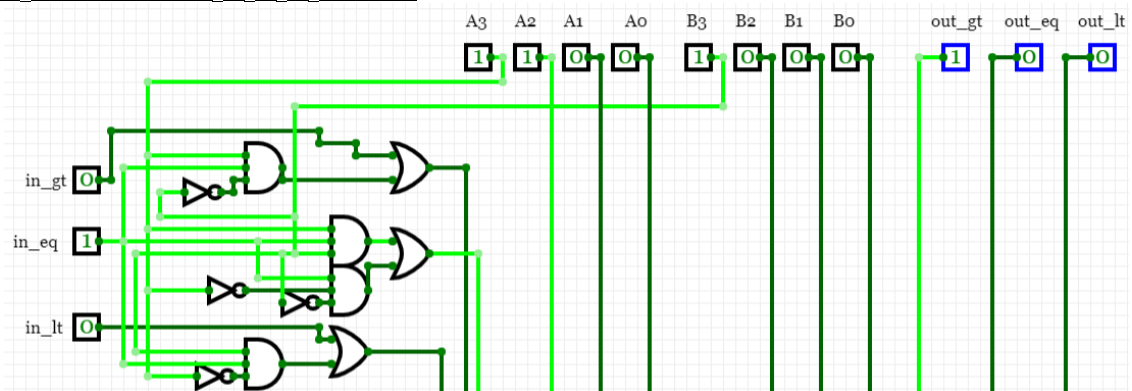
$A_3A_2A_1A_0 = 11xx$ and $B_3B_2B_1B_0 = 10xx$



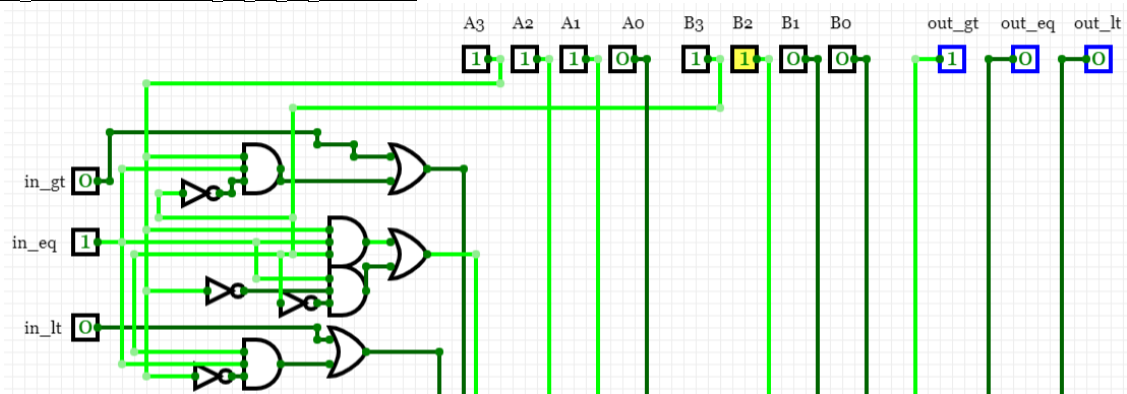$A_3A_2A_1A_0 = 111x$ and $B_3B_2B_1B_0 = 110x$



$A_3A_2A_1A_0 = 1111$ and $B_3B_2B_1B_0 = 1110$

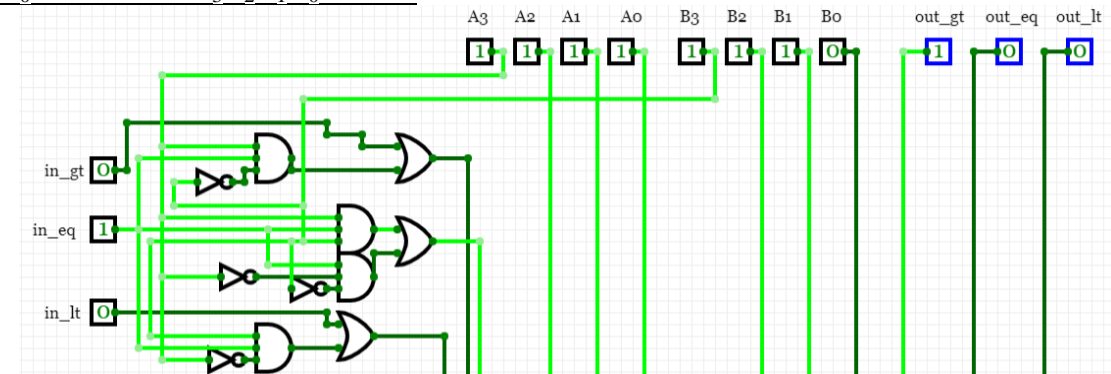

Activity 3.4 — 4-bit Add/Subtract in 2's Complement Representation

A.

For an 8-bit binary number in unsigned representation, the decimal range is $[0, 255]$

For an 8-bit binary number in sign magnitude representation, the decimal range is $[-127, +127]$

For an 8-bit binary number in 2's complement representation, the decimal range is $[-128, +127]$

B.

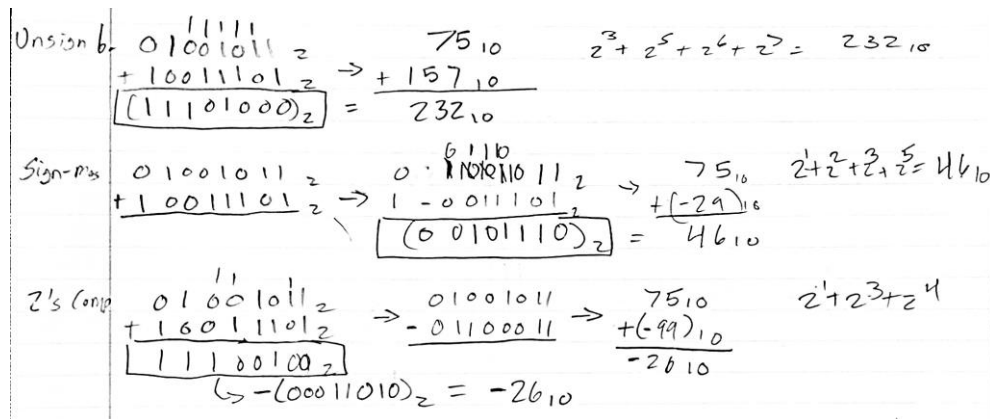


Figure 9: Handwritten work

If the numbers are in unsigned representation $01001011_2 + 10011101_2 = 11101000_2$

If the numbers are in sign magnitude representation $01001011_2 + 10011101_2 = 00101110_2$

If the numbers are in 2's complement representation $01001011_2 + 10011101_2 = 11100100_2$

C.

2's complementation is preferred since it has a slightly larger range which would be a larger benefit at lower bits rather than larger bits since there is a higher probability your sum is on the boundary of your bits if you are at smaller bits. It also helps eliminate the confusion of having two numbers representing zero. Finally, the largest benefit of 2's complement is allowing for the user to use the same hardware for both positive and negative numbers. This is due to the fact that the problems does not have to be changed to a subtraction problem, however the result from the addition may need to be converted to sign magnitude to be in a form that is recognizable since the result of 2's complement edition is in 2's complement.

D.

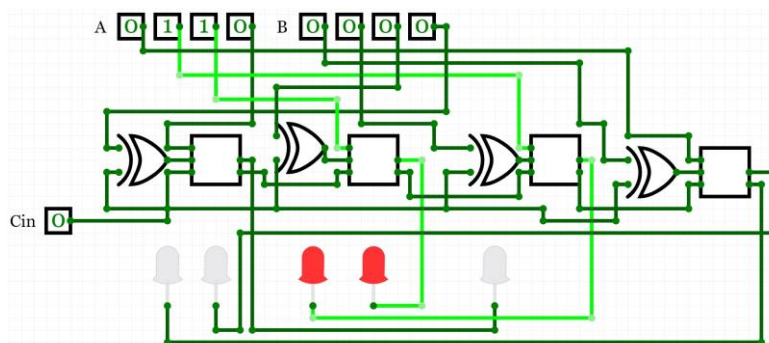


Figure 10: CircuitVerse Diagram of Adder Circuit

 


Figure 11: Circuit With All Outputs At Logic Level 0

 


Figure 12: Circuit Performing 0101 (A) + 0010 (B), Cin = 0

The output was found to be 0 0111 which translates to 3 in decimal which is the expected answer.

 


Figure 13: Circuit Performing 0111 (A) + 1111 (B), Cin = 0

The output was found to be 1 0110 which translates to 6 in decimal which is the expected answer.

 


Figure 14: Circuit Performing 1100 (A) + 1101 (B), Cin = 0

The output was found to be 1 1001 which translates to -7 in decimal which is the expected answer.

To create an output that showcases overflow with A and B both less than 0. To do this, A and B were both chosen to be -5 in decimal, which is 1011.



Figure 15: Circuit Performing 1011 (A) + 1011 (B), Cin = 0

The output was found to be 1 0110 which translates to 6 in decimal, with the removal of the carry, which is not the expected answer showing an overflow error. The expected answer is -10 in decimal and is out of the range for 4-bit binary numbers. Another indication of overflow is the fact that A_3 and B_3 are equal to 1 but $S_3 = 0$ which also shows overflow.



Figure 16: Circuit Performing 0101 (A) - 0010 (B), Cin = 1

The output was found to be 1 0011 which translates to 3 in decimal which is the expected answer.

 


Figure 17: Circuit Performing 0001 (A) - 1010 (B), Cin = 1

The output was found to be 0 0111 which translates to 7 in decimal which is the expected answer.



Figure 18: Circuit Performing 1001 (A) - 1101 (B), Cin = 1

The output was found to be 0 1100 which translates to -4 in decimal which is the expected answer.

To create an output that showcases overflow with A is less than zero and B is greater than zero. To do this, A was chosen to be 1011 which is -5 in decimal and B to be 0101, which is 5 in decimal.



Figure 19: Circuit Performing 1011 (A) - 0101 (B), $C_{in} = 1$

The output was found to be 1 0110 which translates to 6 in decimal, with the removal of the carry, which is not the expected answer showing an overflow error. The expected answer is -10 in decimal and is out of the range for 4-bit binary numbers. Another indication of overflow is the fact that A_3 and B_3 are different and $S_3 = 0$ which also shows overflow.

e.

C_4 is not a good indicator of overflow since C_4 is the carry and since we are adding binary numbers in two's complement there is the chance that we get a carryout that would be discarded in order to get the correct answer. This is the result of taking the two's complement and as such, any carry produced would need to be removed since there is an extra 2^{n+1} that is added when taking the 2's complement.

Two Counter examples:

Counter Example:

$$\begin{array}{r} 7 + (-1) = 6 \\ 0111 \\ + 1111 \\ \hline 10110 \end{array}$$

$C_4 = 1$ but if we disregard the carry we get 0110 which is 6. In decimal, the correct answer.

Counter Example

$$\begin{array}{r} -6 + (-1) = -7 \\ 1010 \\ + 1111 \\ \hline 11001 \end{array}$$

$C_4 = 1$, but if we disregard the carry, we get 1001 which is -7 , the correct answer.

e.

$C_4 \oplus C_3$ is a good indicator of overflow since overflow occurs when both A_3 and B_3 are equal and S_3 is opposite of the input bits. If A_3 and B_3 are equal then S_3 will only equal 1 if C_3 is 1 which will also result in a carry of 1 for C_4 . So if C_3 is equal to zero and A_3 and B_3 are equal, then S_3 will be zero and C_4 will be 1. This is a case of overflow and could be identified with the logic expression $C_4 \oplus C_3$.

Two Examples:

Example:

$$\begin{array}{r} 6 + 4 = 10 \\ 0110 \\ + 0100 \\ \hline 01010 \end{array}$$

Our result 1010, seems correct however this would be a negative number which is impossible when adding two positive numbers. $C_4 = 0$, but $C_3 = 1$. $C_4 \oplus C_3$ would be 1 showing overflow.

Example

$$\begin{array}{r} -5 + -5 = -10 \\ 0101 \\ + 1011 \\ \hline 10110 \end{array}$$

We have overflow since if we removed the carry, our answer would be 0110 which is 6 and not -10. $C_3 = 0$ and $C_4 = 1$. $C_3 \oplus C_4 = 1$ which would correctly identify overflow.

Exercise 3.1 — Mux-Demux Transmission

I started by creating a truth table and formed a form of a truth table that helped me find solution. I made the selection inputs of the demux be the outputs of a logical function involving the first

 


Figure 20: Original Mux to Demux Diagram and Diagram With Added Control Logic

AB	CD
00	00
01	01
10	11
11	10

AB	C	D
00	0	0
01	0	1
10	1	1
11	1	0

$C = A$ $D = A \oplus B$

CD are the control signals of the demux.

Figure 21: Truth Table & K-Map to find the logic for the control signals

By applying the XOR logic gate to the second selector input will result in X_2 activating Y_3 and X_3 activating Y_2 and X_0 and X_1 activating Y_0 and Y_1 respectively.

 


Figure 21: CircuitVerse Implementation To Confirm The Design

Exercise 3.2 — Follow-Up On Activity 3.2

To scale up the circuit in activity 3.2 to be able to count the number of 1's in a 7-bit input, I took the approach of adding onto the original circuit as opposed to incorporating the new bits in the early stages of the circuit. I chose this since approach since I would be more inclined to continue adding onto my original circuit in lab, rather than spending the time to rebuild it. However this methodology may result in using more than materials than necessary. My approach began with adding the additional bits to the least significant bit of the original circuit with a full adder. The sum input becomes the new C_0 and then the carry from the full adder is added to the old C_1 and this process continues with each of order of magnitude until each bit is added. This process results in an extra bit C_3 however it is not necessary for this number of inputs since the total number of 1's of a 7-bit input can be represented by three bits.

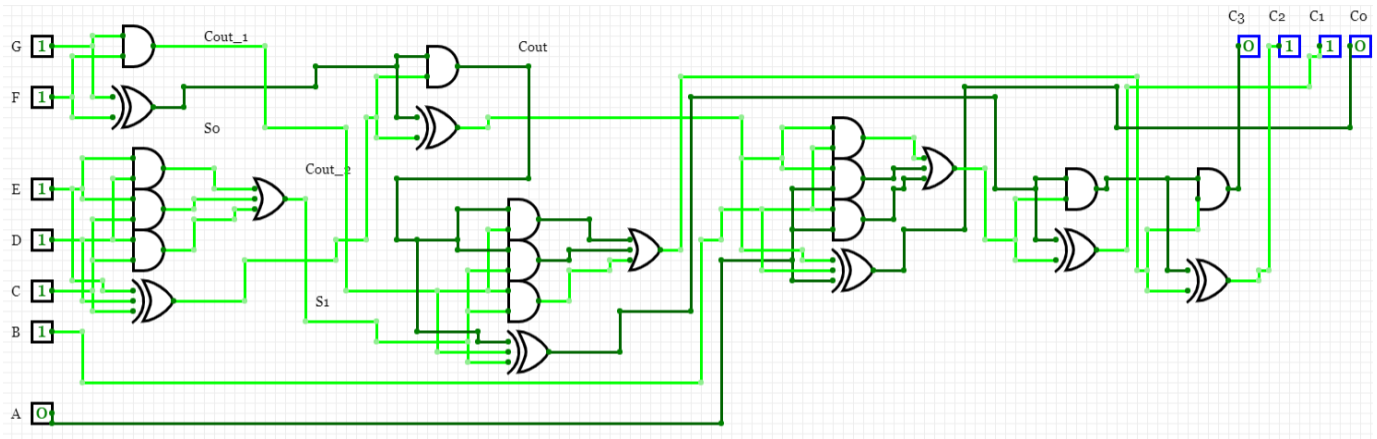


Figure 21: CircuitVerse Implementation Of 7-Bit 1's Adder

Exercise 3.3 - Follow-Up On Activity 3.3

To implement a 4-bit comparator circuit that would detect if a number were greater than 4 and less than or equal to 10, I began with two comparator circuits. I then used an AND gate that would take two inputs, one that said whether the number, n , was greater than 4, and one that said if n was less than or equal to 10. For the input that used that determined if the number was greater than 4, I connected the greater than output to the AND gate. For the other input I used the out_eq and out_lt outputs and put them through an OR gate and then put the output into the final AND gate. The output of this AND gate would be at logic level one if both the number were greater than 4 or less than or equal to 10. To simplify the circuit, I began removing the outputs that I did not use which allowed for me to remove portions of the circuit that did not affect the output I needed. The downside that I can foresee is that this circuit will only be useful for this application and would not be easily changed for another application, however this implementation uses far less gates.



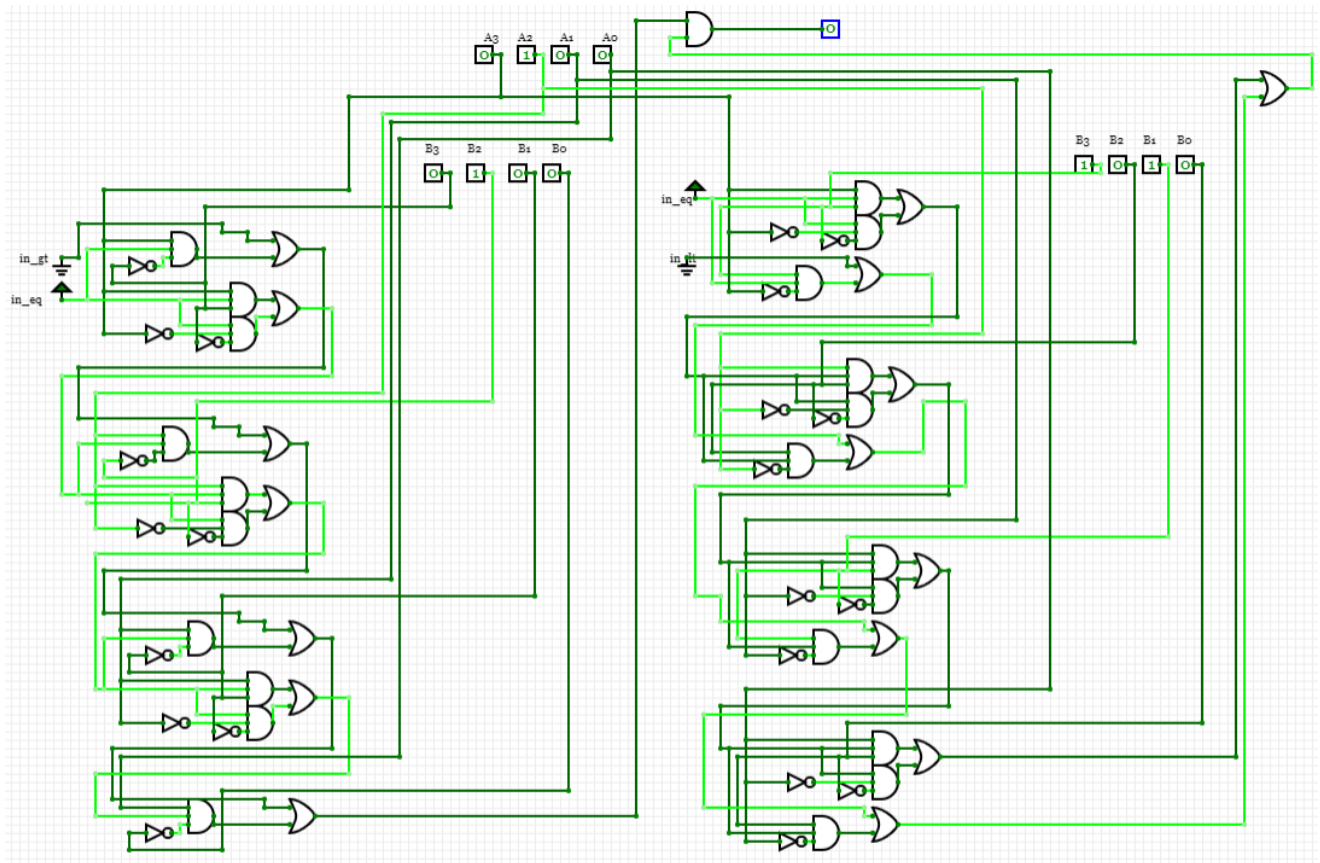
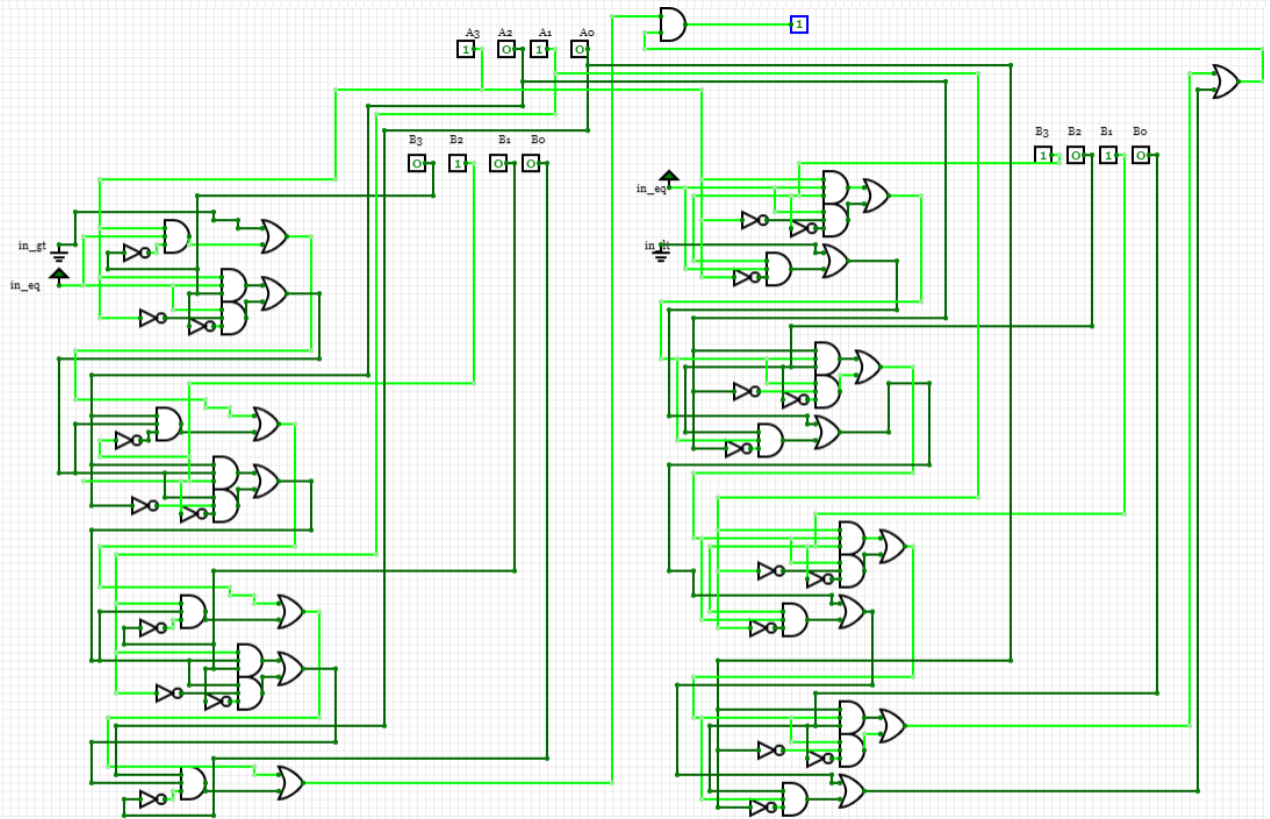


Figure 22: CircuitVerse Implementation Of Comparator With Various Inputs

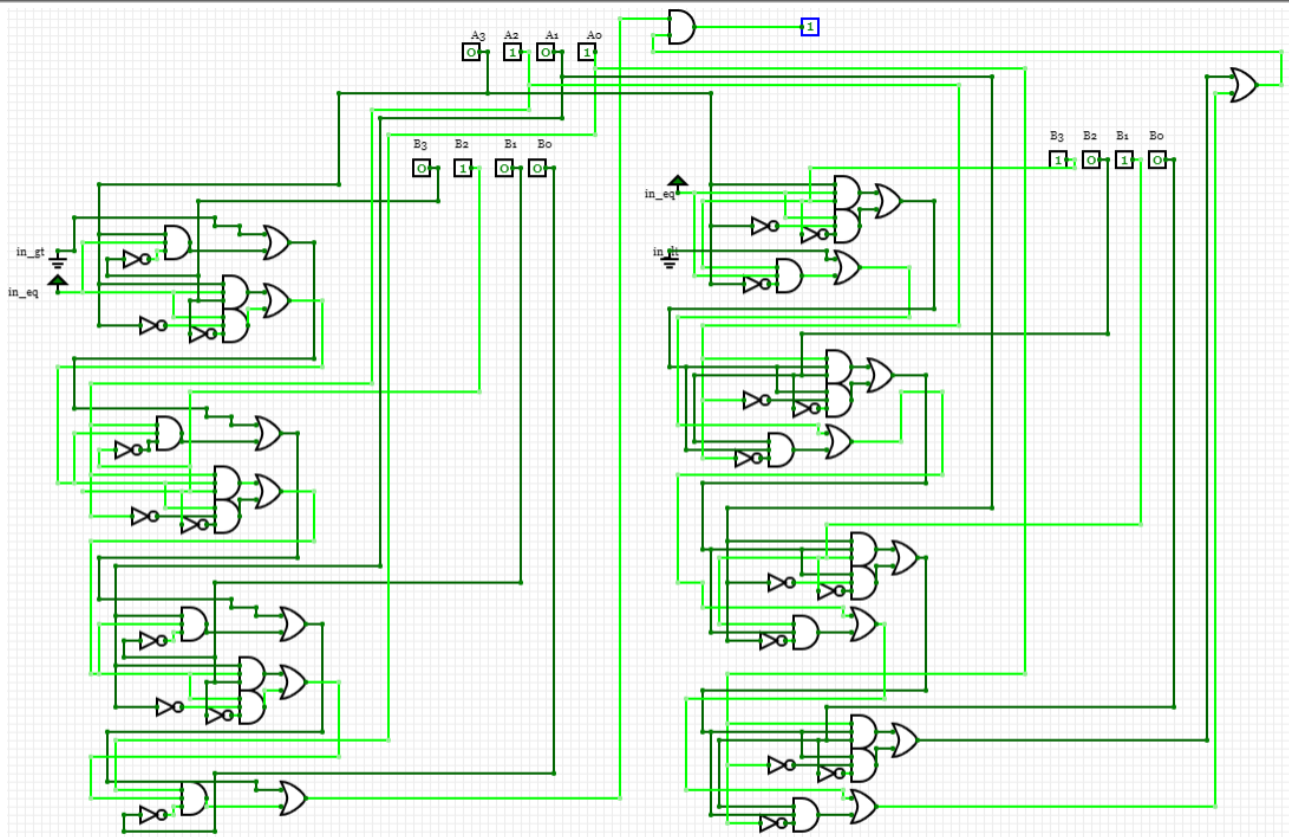

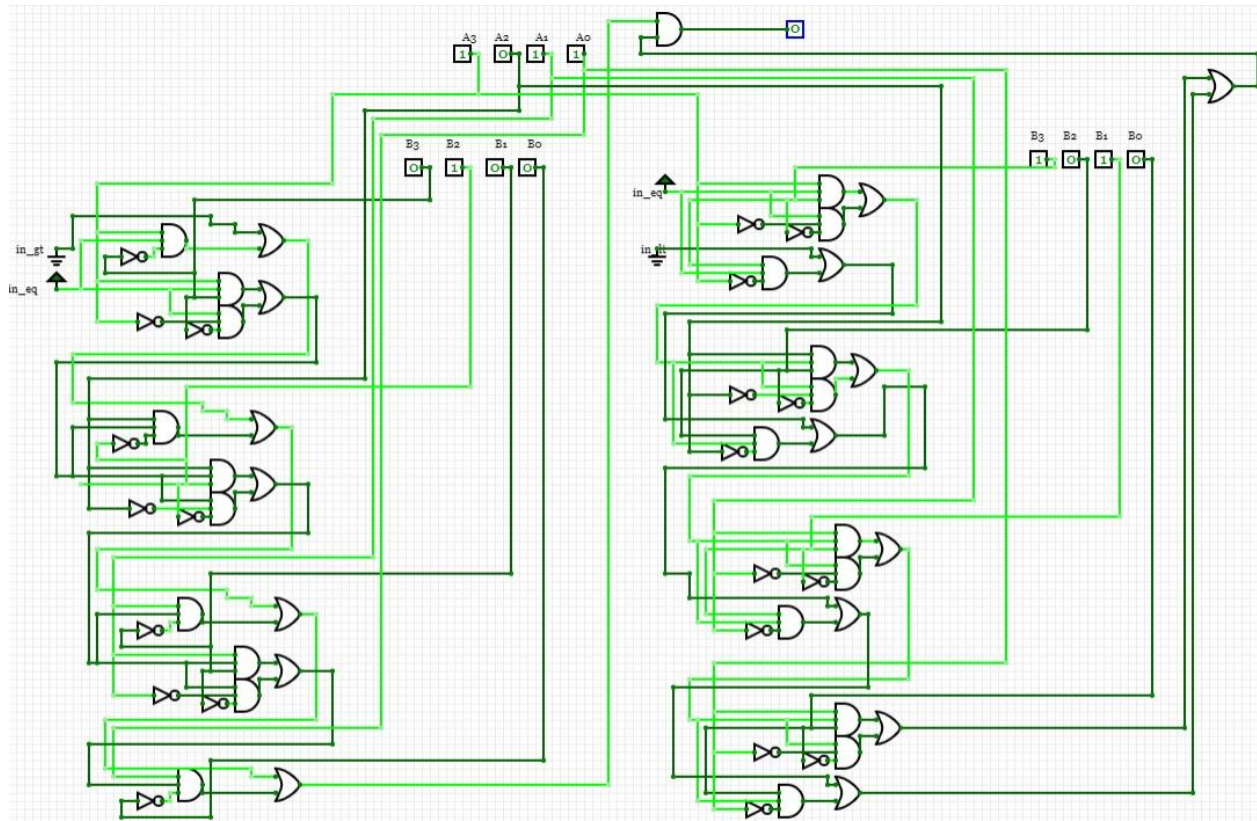

Exercise 3.4 - Follow-Up On Activity 3.4

A.

The two general cases when we have overflow are when A_3 and B_3 are both zero and S_3 is one which implies that C_3 is one but C_4 is zero since the addition of 0 and 1 does not produce a carry. The other case where overflow occurs is when A_3 and B_3 are both one and S_3 is zero which implies that C_3 is zero and C_4 is one since the addition of 1 and 1 produces a carry.

B.

To implement overflow detection with the 74LS283 we would use the logic function $O(A_3, B_3, S_3) = A_3 B_3 S_3' + (A_3)' (B_3)' S_3$ which incorporates both general cases where overflow occurs.

 


Figure 23: Logic Diagram To Determine Overflow.